 



HOMEWORK 2.**Due: Monday, April 4, 2022.****This is an individual assignment!****1. Delays**

Consider an inverter driving a capacitive load in ASAP7 technology.



All transistors have $W/L = 12$, $V_{DD} = 0.75V$. In this technology, you can assume that $C_g = C_d = 2\text{fF}/\mu\text{m}$, transistor thresholds are $0.3V$ and fanout-of-4 inverter delay is 12ps .

- For what range of sizes of the load capacitor, C_L , adding another inverter to drive the load reduces the delay?
- If the input capacitance of the first inverter in the figure below is set to $C_1 = 1.5\text{fF}$, the wire capacitance C_w is 1fF , how would you size the second inverter that is driving 17.5fF load to minimize the overall delay from In to Out ? Is this result intuitive?

 **2. Latch timing**

A timing path with a single register driving a latch-based system is shown in Figure 2. R0 is a rising-edge triggered register, while R1, R2, and R3 are level sensitive. There are two 50% duty cycle clock phases available, with clkb offset from clk by half a period. Both registers and latches have zero hold time, and there is no clock skew in the system. Registers have $t_{\text{clk-Q}} = 100\text{ps}$. Latches have $t_{\text{clk-Q}} = t_{\text{D-Q}} = t_{\text{su}} = 150\text{ps}$.

 


Figure 2.

- The critical path of S1 is 600 ps, the critical path of S2 is 400 ps, and the critical path of S3 is 550 ns. Compute the minimum clock period.
- Assume that we can model the on current with $I_{on} = K(V_{DD} - V_{thz})$, with $K = 0.002$, $V_{DD} = 0.75$ V, and $V_{thz} = 0.3$ V. There is a systematic variation on V_{thz} . What is the maximum value of V_{thz} that leads to a 15% increase in delay?
- The systematic variation of V_{thz} is normally distributed with $\sigma = 0.05$ V. What would be the yield in terms of timing if you are allowed a 15% margin on the clock period?

3. Flip-Flop

A flip-flop is shown in Figure 3.

 


Figure 2.

In this process, a symmetrically sized inverter has $W_p = W_n$, and a unit-sized transistor has gate and drain capacitances of 1fF and the on-resistance of 2.5kΩ. The resistance of a stack of two devices is 1.5x of the resistance of a single transistor with the same width. You can assume that the true and complementary clocks are ideal, and the logical effort of creating \overline{Clk} from Clk is 1.

- Is the flip-flop triggered by a rising or a falling edge of the Clk ?
- Calculate the $Clk - \overline{Q}$ delay for a 0→1 transition at the output and show your work.
- Calculate the hold time for $D = 1$.