 



**HOMEWORK 2.****Due: Monday, April 4, 2022.****This is an individual assignment!****1. Delays**

Consider an inverter driving a capacitive load in ASAP7 technology.



All transistors have  $W/L = 12$ ,  $V_{DD} = 0.75V$ . In this technology, you can assume that  $C_g = C_d = 2\text{fF}/\mu\text{m}$ , transistor thresholds are  $0.3V$  and fanout-of-4 inverter delay is  $12\text{ps}$ .

- For what range of sizes of the load capacitor,  $C_L$ , adding another inverter to drive the load reduces the delay?
- If the input capacitance of the first inverter in the figure below is set to  $C_1 = 1.5\text{fF}$ , the wire capacitance  $C_w$  is  $1\text{fF}$ , how would you size the second inverter that is driving  $17.5\text{fF}$  load to minimize the overall delay from  $In$  to  $Out$ ? Is this result intuitive?

 **2. Latch timing**

A timing path with a single register driving a latch-based system is shown in Figure 2. R0 is a rising-edge triggered register, while R1, R2, and R3 are level sensitive. There are two 50% duty cycle clock phases available, with  $\text{clkb}$  offset from  $\text{clk}$  by half a period. Both registers and latches have zero hold time, and there is no clock skew in the system. Registers have  $t_{\text{clk-Q}} = 100\text{ps}$ . Latches have  $t_{\text{clk-Q}} = t_{\text{D-Q}} = t_{\text{su}} = 150\text{ps}$ .

 


Figure 2.

- The critical path of S1 is 600 ps, the critical path of S2 is 400 ps, and the critical path of S3 is 550 ps. Compute the minimum clock period.
- Assume that we can model the on current with  $I_{on} = K(V_{DD} - V_{thz})$ , with  $K = 0.002$ ,  $V_{DD} = 0.75$  V, and  $V_{thz} = 0.3$  V. There is a systematic variation on  $V_{thz}$ . What is the maximum value of  $V_{thz}$  that leads to a 15% increase in delay?
- The systematic variation of  $V_{thz}$  is normally distributed with  $\sigma = 0.05$  V. What would be the yield in terms of timing if you are allowed a 15% margin on the clock period?

### 3. Flip-Flop

A flip-flop is shown in Figure 3.

 


Figure 2.

In this process, a symmetrically sized inverter has  $W_p = W_n$ , and a unit-sized transistor has gate and drain capacitances of 1fF and the on-resistance of 2.5kΩ. The resistance of a stack of two devices is 1.5x of the resistance of a single transistor with the same width. You can assume that the true and complementary clocks are ideal, and the logical effort of creating  $\overline{Clk}$  from  $Clk$  is 1.

- Is the flip-flop triggered by a rising or a falling edge of the  $Clk$ ?
- Calculate the  $Clk - \overline{Q}$  delay for a 0→1 transition at the output and show your work.
- Calculate the hold time for  $D = 1$ .